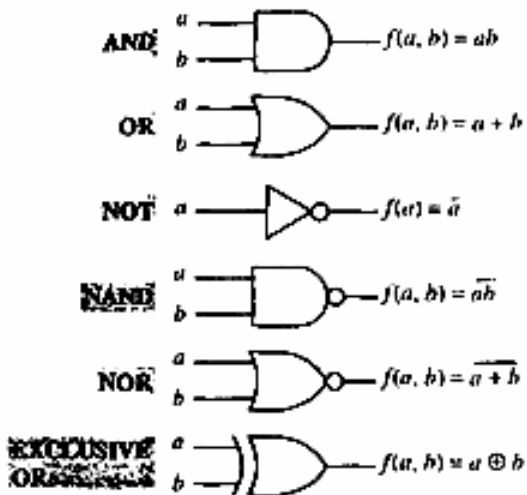



# Algebraic and Synthesis (Cont.)

## Electronic Logic Gates

### Gate Symbols




Symbol set 1

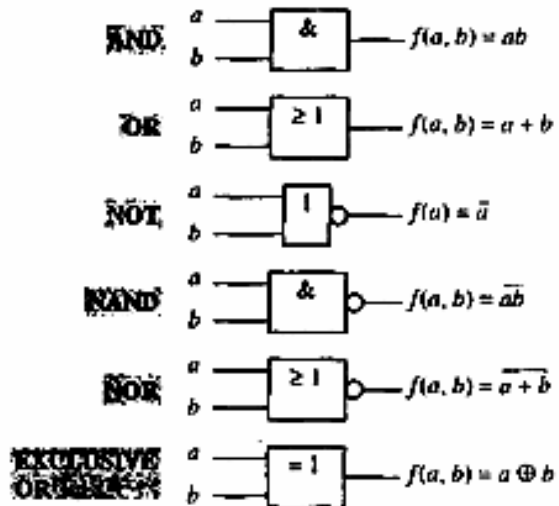


1

## Electronic Logic Gates

 

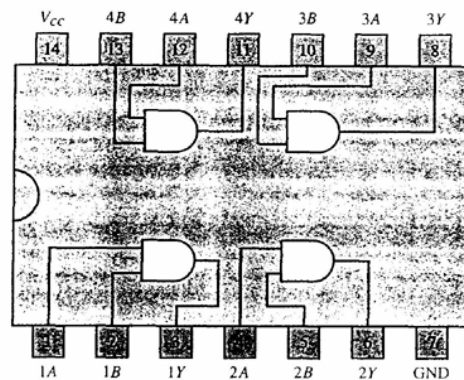7402:  $Y = \overline{A + B}$   
Quadrate two-input NOR gates



7408:  $Y = AB$   
Quadrate two-input AND gates

2

# Electronic Logic Gates


## Basic Function Component

| $a$ | $f_{NOT}(a) = \bar{a}$ |
|-----|------------------------|
| 0   | 1                      |
| 1   | 0                      |

(a)

| $A$ | $Y$ |
|-----|-----|
| L   | H   |
| H   | L   |

(b)

 

(c)




(d)

| $a$ | $b$ | $f_{AND}(a, b) = ab$ |
|-----|-----|----------------------|
| 0   | 0   | 0                    |
| 0   | 1   | 0                    |
| 1   | 0   | 0                    |
| 1   | 1   | 1                    |


(a)

| $A$ | $B$ | $Y$ |
|-----|-----|-----|
| L   | L   | L   |
| L   | H   | L   |
| H   | L   | L   |
| H   | H   | H   |

(b)

 

(c)

 

(d)

# Electronic Logic Gates

## Basic Function Component

| $a$ | $b$ | $f_{OR}(a, b) = a + b$ |
|-----|-----|------------------------|
| 0   | 0   | 0                      |
| 0   | 1   | 1                      |
| 1   | 0   | 1                      |
| 1   | 1   | 1                      |


(a)

| $A$ | $B$ | $Y$ |
|-----|-----|-----|
| L   | L   | L   |
| L   | H   | H   |
| H   | L   | H   |
| H   | H   | H   |

(b)



(c)

 

(d)

| $a$ | $b$ | $\text{sum}(a, b)$ | $\text{sum}(a, b) \geq 1?$ | $f_{OR}(a, b) = a + b$ |
|-----|-----|--------------------|----------------------------|------------------------|
| 0   | 0   | 0                  | False                      | 0                      |
| 0   | 1   | 1                  | True                       | 1                      |
| 1   | 0   | 1                  | True                       | 1                      |
| 1   | 1   | 2                  | True                       | 1                      |

# Electronic Logic Gates

- Positive VS. Negative Logic

$$\begin{aligned}y &= a \cdot b \\ &= \overline{\overline{a \cdot b}} \\ &= \overline{\bar{a} + \bar{b}} \\ &= \bar{f}_{OR}(\bar{a}, \bar{b})\end{aligned}$$



5

# Electronic Logic Gates

- Positive VS. Negative Logic

$$\begin{aligned}y &= a + b \\ &= \overline{\overline{a + b}} \\ &= \overline{\bar{a} \cdot \bar{b}} \\ &= \bar{f}_{AND}(\bar{a}, \bar{b})\end{aligned}$$



(b)

6

# Electronic Logic Gates

## ■ NAND Gates

| $a$ | $b$ | $f_{\text{NAND}}(a, b) = \overline{ab}$ |
|-----|-----|---|
| 0   | 0   | 1                                       |
| 0   | 1   | 1                                       |
| 1   | 0   | 1                                       |
| 1   | 1   | 0                                       |

(a)

| $A$ | $B$ | $Y$ |
|-----|-----|-----|
| L   | L   | H   |
| L   | H   | H   |
| H   | L   | H   |
| H   | H   | L   |

(b)



(c)



(d)



(e)


7

# Electronic Logic Gates

$$f_{\text{NAND}}(a, a) = \overline{a \cdot a} = \bar{a} = f_{\text{NOT}}(a)$$


$$\overline{\overline{a \cdot b}} = a \cdot b = f_{\text{AND}}(a, b)$$
 
$$f_{\text{NAND}}(\bar{a}, \bar{b}) = \overline{\bar{a} \cdot \bar{b}} = a + b = f_{\text{OR}}(a, b)$$



AND gate

NOT gate

 

OR gate

8

# Electronic Logic Gates

## ■ NOR Gates

| $a$ | $b$ | $f_{\text{NOR}}(a, b) = \overline{a + b}$ |
|-----|-----|---|
| 0   | 0   | 1   |
| 0   | 1   | 0   |
| 1   | 0   | 0   |
| 1   | 1   | 0   |

(a)

| $A$ | $B$ | $Y$ |
|-----|-----|-----|
| L   | L   | H   |
| L   | H   | L   |
| H   | L   | L   |
| H   | H   | L   |

(b)





9

# Electronic Logic Gates

$$f_{\text{NOR}}(a, a) = \overline{a + a} = \bar{a} = f_{\text{NOT}}(a)$$

$$\overline{f_{\text{NOR}}(a, b)} = \overline{\overline{a + b}} = a + b = f_{\text{OR}}(a, b)$$
  
$$f_{\text{NOR}}(\bar{a}, \bar{b}) = \overline{\bar{a} + \bar{b}} = a \cdot b = f_{\text{AND}}(a, b)$$



AND gate

10

# Electronic Logic Gates

## Exclusive OR Gates (XOR Gates)

| $a$ | $b$ | $f_{XOR}(a, b) = a \oplus b$ |
|-----|-----|------------------------------|
| 0   | 0   | 0                            |
| 0   | 1   | 1                            |
| 1   | 0   | 1                            |
| 1   | 1   | 0                            |


(a)

| $A$ | $B$ | $Y$ |
|-----|-----|-----|
| L   | L   | L   |
| L   | H   | H   |
| H   | L   | H   |
| H   | H   | L   |

(b)



(c)

 

(d)

$$a \oplus b = \bar{a}b + a\bar{b}$$

$$= \bar{a}a + \bar{a}b + a\bar{b} + b\bar{b}$$

$$= \bar{a}(a + b) + \bar{b}(a + b)$$

$$= (\bar{a} + \bar{b})(a + b)$$

[P2(a), P6(b)]

[P5(b)]

[P5(b)]

$$a \oplus a = 0$$

$$a \oplus \bar{a} = 1$$

$$a \oplus 0 = a$$

$$a \oplus 1 = \bar{a}$$

# Electronic Logic Gates

$$a \oplus a = 0$$

$$a \oplus \bar{a} = 1$$

$$a \oplus 0 = a$$

$$a \oplus 1 = \bar{a}$$

| $a$ | $b$ | $sum(a, b)$ | $sum(a, b) = 1?$ | $f(a, b) = a \oplus b$ |
|-----|-----|-------------|------------------|------------------------|
| 0   | 0   | 0           | False            | 0                      |
| 0   | 1   | 1           | True             | 1                      |
| 1   | 0   | 1           | True             | 1                      |
| 1   | 1   | 2           | False            | 0                      |

# Electronic Logic Gates

- Exclusive NOR Gates (XNOR Gates)

| $a$ | $b$ | $f_{XNOR}(a, b) = a \odot b$ |
|-----|-----|------------------------------|
| 0   | 0   | 1                            |
| 0   | 1   | 0                            |
| 1   | 0   | 0                            |
| 1   | 1   | 1                            |


(a)

| $A$ | $B$ | $Y$ |
|-----|-----|-----|
| L   | L   | H   |
| L   | H   | L   |
| H   | L   | L   |
| H   | H   | H   |

(b)



(c)

 

(d)

$$\begin{aligned} a \odot b &= \overline{a \oplus b} \\ &= \overline{\bar{a}b + a\bar{b}} \\ &= \overline{\bar{a}b} \cdot \overline{a\bar{b}} \end{aligned}$$

$$\begin{aligned} &= (a + \bar{b})(\bar{a} + b) \\ &= a\bar{a} + ab + \bar{a}\bar{b} + \bar{b}b \\ &= ab + \bar{a}\bar{b} \end{aligned}$$

It can also be easily verified that

$$a \oplus \bar{b} = a \odot b$$

# Analysis of Combinational Circuits

- Algebraic Methods

$$P_1 = \overline{ab}$$

$$P_2 = \overline{\bar{a} + c}$$

$$P_3 = b \oplus \bar{c}$$

$$P_4 = P_1 \cdot P_2 = \overline{ab} \cdot \overline{(\bar{a} + c)}$$

$$\begin{aligned} f(a, b, c) &= \overline{P_3 + P_4} \\ &= \overline{(b \oplus \bar{c}) + \overline{ab} \cdot \overline{(\bar{a} + c)}} \end{aligned}$$

$$\bar{f}(a, b, c) = (b \oplus \bar{c}) + \overline{ab} \cdot \overline{\bar{a} + c}$$

$$= bc + \bar{b}\bar{c} + \overline{ab} \cdot \bar{a} + c$$

$$= bc + \bar{b}\bar{c} + (\bar{a} + \bar{b})a\bar{c}$$


$$= bc + \bar{b}\bar{c} + a\bar{b}\bar{c}$$

$$= bc + \bar{b}\bar{c}$$

$$\bar{f}(a, b, c) = b \odot c$$

$$f(a, b, c) = \overline{b \odot c} = b \oplus c$$

# Analysis of Combinational Circuits

 

15


# Analysis of Combinational Circuits

$$\begin{aligned}
 f(a, b, c) &= \overline{(a \oplus b)(b \oplus c)} \cdot (\overline{\bar{a} + \bar{b} + a + c}) \\
 &= \overline{(a \oplus b)(b \oplus c)} + \bar{a} + \bar{b} + a + c \\
 &= (a \oplus b)(b \oplus c) + (\bar{a} + \bar{b})(a + c) \\
 &= (a\bar{b} + \bar{a}b)(b\bar{c} + \bar{b}c) + (\bar{a} + \bar{b})(a + c) \\
 &= a\bar{b}\bar{c} + a\bar{b}c + \bar{a}b\bar{c} + \bar{a}bc + \bar{a}a + \bar{a}c + a\bar{b} + \bar{b}c \\
 &= a\bar{b}\bar{c} + \bar{a}b\bar{c} + \bar{a}c + a\bar{b} + \bar{b}c \\
 &= \bar{a}b\bar{c} + \bar{a}c + a\bar{b} \\
 &= \bar{a}b + \bar{a}c + a\bar{b} \\
 &= \bar{a}c + a \oplus b
 \end{aligned}$$

16



# Analysis of Combinational Circuits

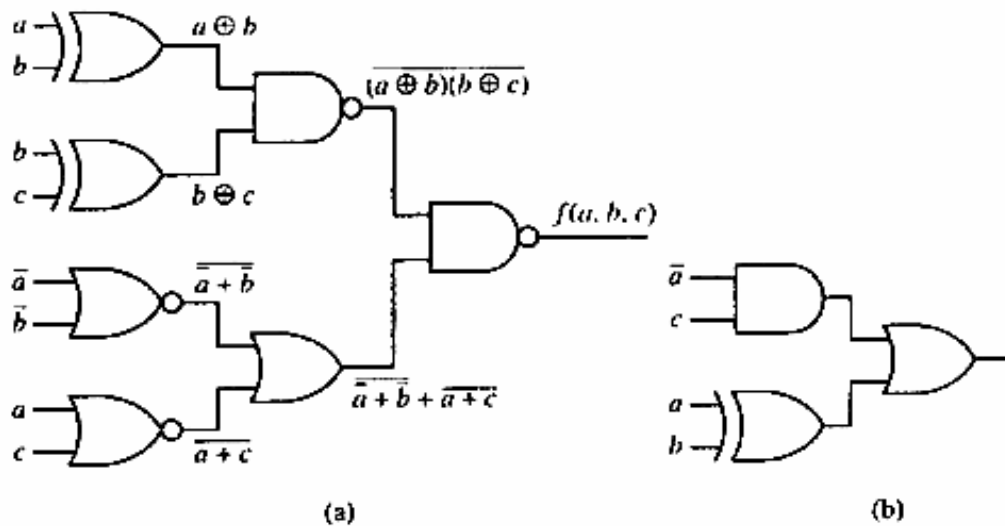

17

# Analysis of Combinational Circuits

- Truth Table Methods

| $abc$ | $\bar{a}c$ | $a \oplus b$ | $f(a, b, c)$ |
|-------|------------|--------------|--------------|
| 000   | 0          | 0            | 0            |
| 001   | 1          | 0            | 1            |
| 010   | 0          | 1            | 1            |
| 011   | 1          | 1            | 1            |
| 100   | 0          | 1            | 1            |
| 101   | 0          | 1            | 1            |
| 110   | 0          | 0            | 0            |
| 111   | 0          | 0            | 0            |

18

# Analysis of Combinational Circuits

## ■ Timing Diagram


- : is a graphic representation of input and output signal relationship in switching network.

$$\begin{aligned} f_{\alpha}(A, B, C) &= \sum m(1, 2, 6, 7) \\ &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + AB\bar{C} + ABC \\ &= \bar{A}\bar{B}C + B\bar{C} + AB \end{aligned}$$

$$\begin{aligned} f_{\beta}(A, B, C) &= \sum m(1, 3, 5, 6) \\ &= \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}C + ABC \\ &= \bar{A}C + A\bar{B}C + ABC \end{aligned}$$

19

# Analysis of Combinational Circuits

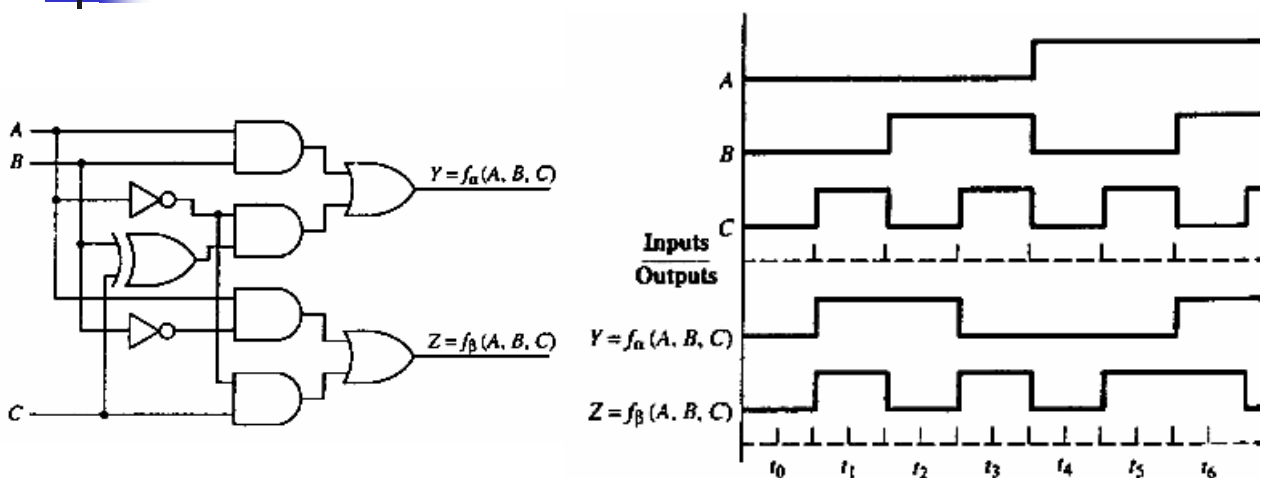

20

# Analysis of Combinational Circuits

| Time  | Inputs | Outputs        |                |
|-------|--------|----------------|----------------|
|       | ABC    | $f_a(A, B, C)$ | $f_b(A, B, C)$ |
| $t_0$ | 000    | 0              | 0              |
| $t_1$ | 001    | 1              | 1              |
| $t_2$ | 010    | 1              | 0              |
| $t_3$ | 011    | 0              | 1              |
| $t_4$ | 100    | 0              | 0              |
| $t_5$ | 101    | 0              | 1              |
| $t_6$ | 110    | 1              | 1              |
| $t_7$ | 111    | 1              | 0              |

21

# Analysis of Combinational Circuits

## ■ Propagation Delays

- The Delay between time of a input change and the corresponding output change.

$t_{PLH}$  = propagation delay time, low- to high-level output


$t_{PHL}$  = propagation delay time, high- to low-level output

- Single propagation delay parameter,  $t_{PD}$

$$t_{PD} = \frac{t_{PLH} + t_{PHL}}{2}$$

22

# Analysis of Combinational Circuits

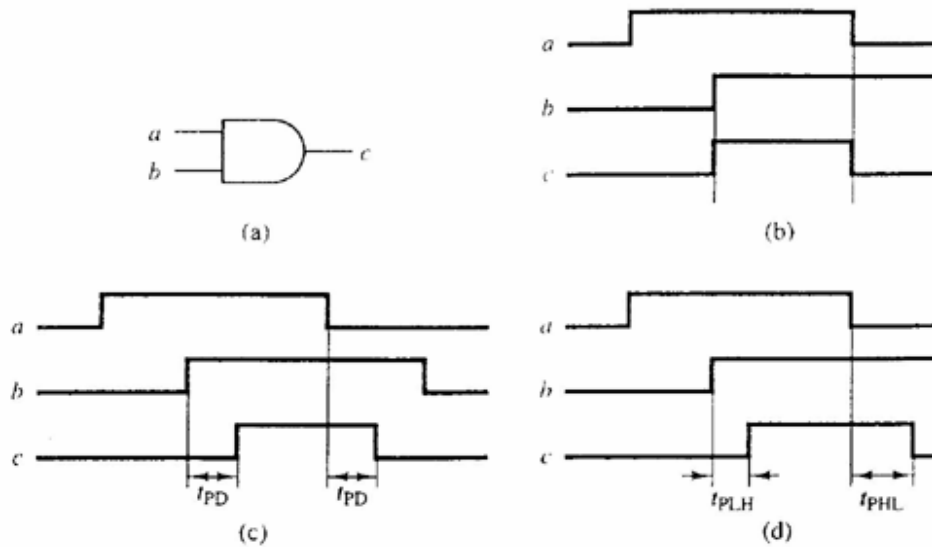


23

# Analysis of Combinational Circuits

| Logic Family | Propagation Delay | Power Dissipation |
|--------------|-------------------|-------------------|
|              | $t_{PD}$ (ns)     | Per Gate (mW)     |
| 7400         | 10                | 10                |
| 74H00        | 6                 | 22                |
| 74L00        | 33                | 1                 |
| 74LS00       | 9.5               | 2                 |
| 74S00        | 3                 | 19                |
| 74ALS00      | 3.5               | 1.3               |
| 74AS00       | 3                 | 8                 |
| 74HC00       | 8                 | 0.17              |

24


# Analysis of Combinational Circuits

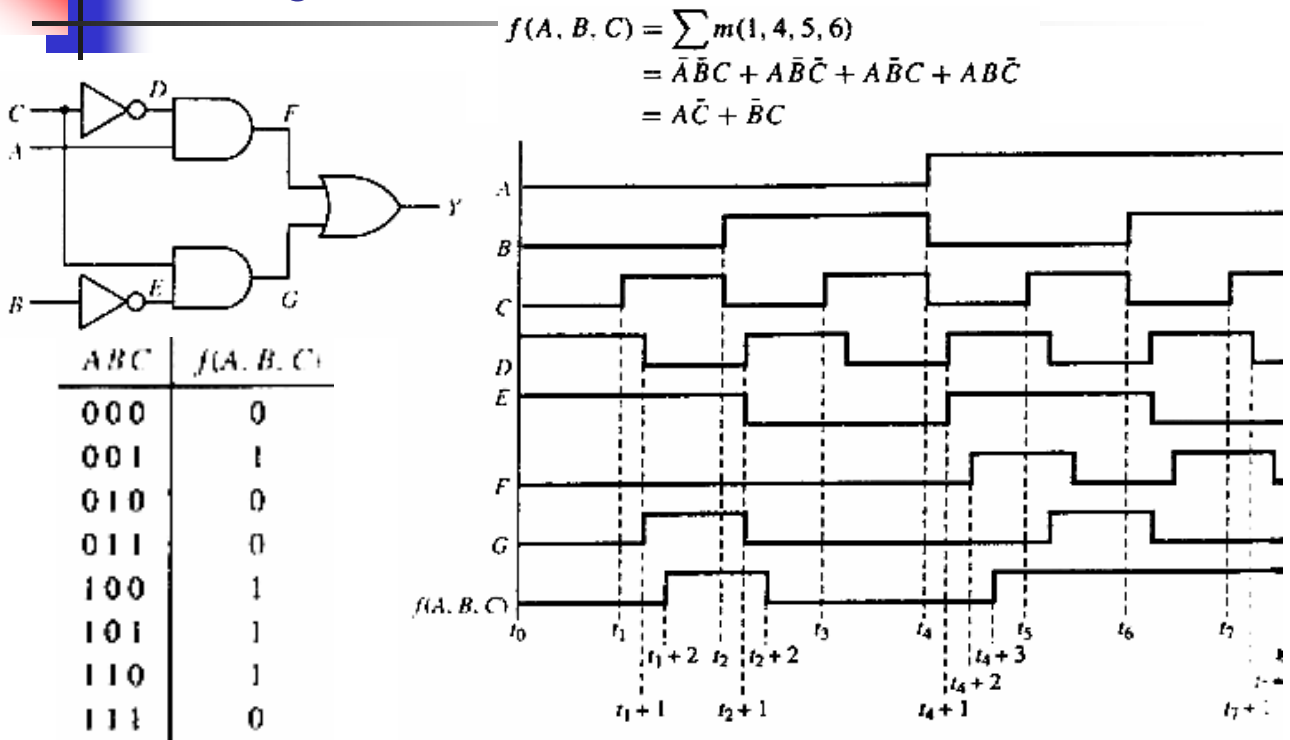
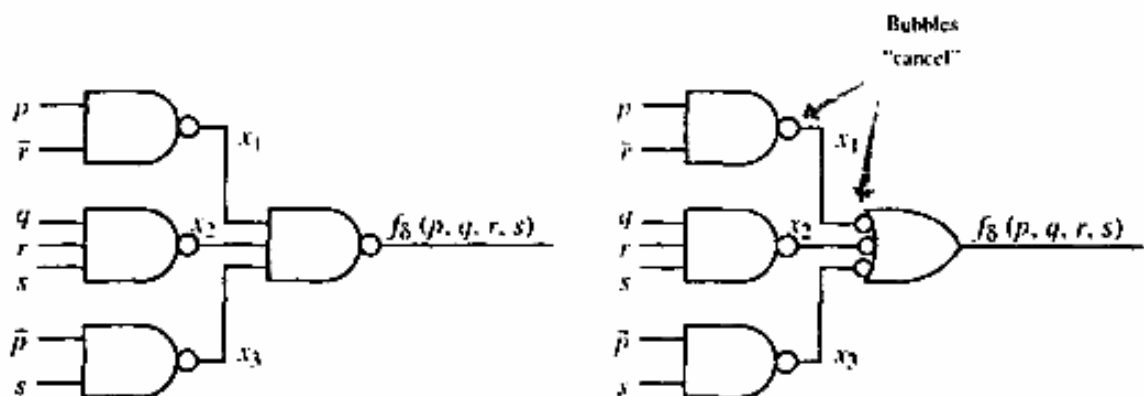
# Synthesis of Combinational Logic Circuit

- AND-OR and NAND Networks




$$f_8(p, q, r, s) = p\bar{r} + qrs + \bar{p}s$$


   
# Synthesis of Combinational Logic Circuit

- OR-AND and NOR Networks



$$f_c(A, B, C, D) = (\bar{A} + B + C)(B + C + D)(\bar{A} + D)$$



27

# Synthesis of Combinational Logic Circuit




- Two Level Network

  

28

# Synthesis of Combinational Logic Circuit

$$f(a, b, c, d, e) = abcde$$

   

29

# Synthesis of Combinational Logic Circuit


- Implement in NAND or NOR Logic
  - STEP 1: Express the function in minterm (maxterm) list form.
  - STEP 2: Write out the minterm (maxterm) in algebraic form.
  - STEP 3: Simplify the function in SOP (POS) form.
  - STEP 4: Use Theorem 8a(8b) and T3 to transform the expression into the NAND (NOR) form.
  - STEP 5: Draw the NAND (NOR) logic diagram.

30

# Synthesis of Combinational Logic Circuit

Implement  $f_\phi(X, Y, Z) = \sum m(0, 3, 4, 5, 7)$  in NAND logic.

 1.  $f_\phi(X, Y, Z) = \sum m(0, 3, 4, 5, 7)$
2.  $f_\phi(X, Y, Z) = m_0 + m_3 + m_4 + m_5 + m_7$   
 $= \bar{X}\bar{Y}\bar{Z} + \bar{X}YZ + X\bar{Y}\bar{Z} + X\bar{Y}Z + XYZ$
3.  $f_\phi(X, Y, Z) = \bar{Y}\bar{Z} + YZ + XZ$  [T6(a)]
- 4a.  $f_\phi(X, Y, Z) = \overline{\bar{Y}\bar{Z}} + \overline{YZ} + \overline{XZ}$  [T3]
- or
- 4b.  $f_\phi(X, Y, Z) = \overline{\bar{Y}\bar{Z} + YZ + XZ}$  [T3]  
 $= \overline{\bar{Y}\bar{Z}} \cdot \overline{YZ} \cdot \overline{XZ}$  [T8(a)]




31

# Synthesis of Combinational Logic Circuit

Implement  $f_\phi(X, Y, Z) = \sum m(0, 3, 4, 5, 7)$  in NOR logic.

 1.  $f_\phi(X, Y, Z) = \prod M(1, 2, 6)$
2.  $f_\phi(X, Y, Z) = M_1 \cdot M_2 \cdot M_6$   
 $= (X + Y + \bar{Z})(X + \bar{Y} + Z)(\bar{X} + \bar{Y} + Z)$
3.  $f_\phi(X, Y, Z) = (X + Y + \bar{Z})(\bar{Y} + Z)$  [T6(b)]
- 4a.  $f_\phi(X, Y, Z) = \overline{(X + Y + \bar{Z}) \cdot (\bar{Y} + Z)}$  [T3]
- or
- 4b.  $f_\phi(X, Y, Z) = \overline{(X + Y + \bar{Z})(\bar{Y} + Z)}$  [T3]  
 $= \overline{(X + Y + \bar{Z})} + \overline{(\bar{Y} + Z)}$  [T8(b)]




32



# Synthesis of Combinational Logic Circuit

- AOI Circuit (AND-OR-INVERT)

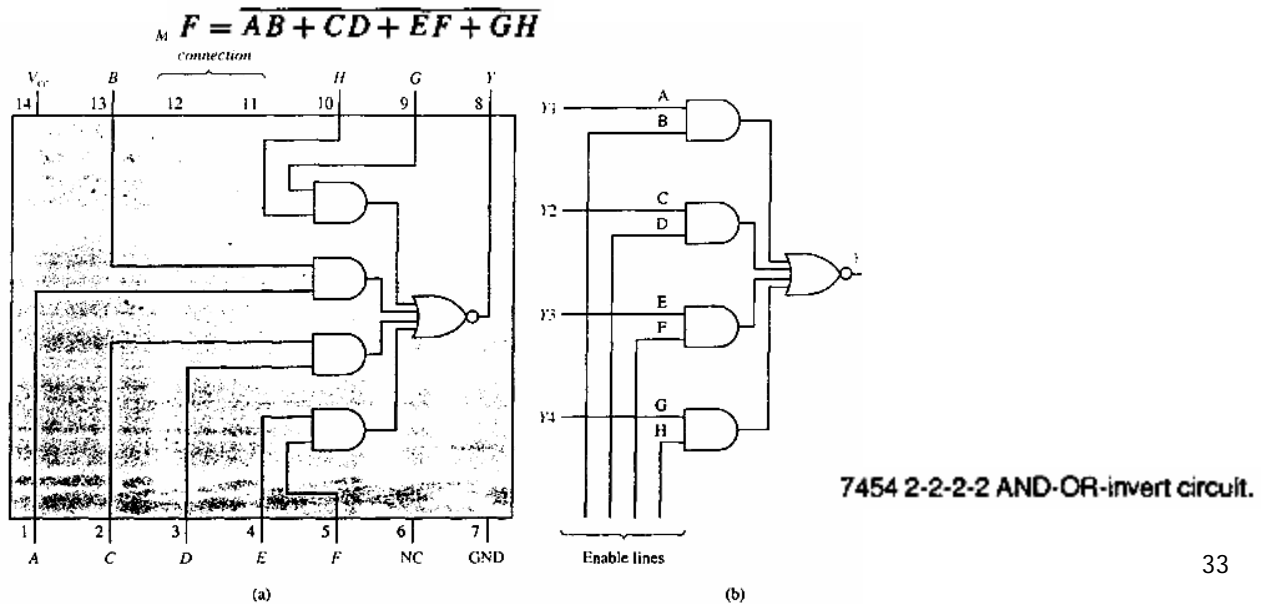

33

# Synthesis of Combinational Logic Circuit

- Factoring

- Factoring is a technique for obtaining higher-level form of switching function.
- For require less hardware.
- For more economical to implement.
- For limited fan-in must be used.



34

# Synthesis of Combinational Logic Circuit

Suppose we are given the following four-variable function:

$$f_2(A, B, C, D) = A\bar{B} + A\bar{D} + A\bar{C}$$
  
$$\begin{aligned} f_1(A, B, C, D) &= A\bar{B} + A\bar{D} + A\bar{C} \\ &= A(\bar{B} + \bar{D} + \bar{C}) \\ &= A(\overline{BCD}) \end{aligned}$$



35


# Synthesis of Combinational Logic Circuit

Realize the function  $f(a, b, c, d) = \sum m(8, 13)$  using only two-input AND and OR gates.

We begin by writing the canonical SOP form:

$$\begin{aligned} f(a, b, c, d) &= \sum m(8, 13) \\ &= a\bar{b}\bar{c}\bar{d} + ab\bar{c}d \end{aligned}$$
 
$$\begin{aligned} f(a, b, c, d) &= a\bar{b}\bar{c}\bar{d} + ab\bar{c}d \\ &= (a\bar{c})(\bar{b}\bar{d} + b\bar{c}d) \end{aligned}$$



36