



# Modular Combinational Logic

---

1



## Agenda


---

- Decoder
- Encoder
- Multiplexers / Data Selectors
- Demultiplexers / Data Distributors

2
 
# Decoder



- Decoder is a multiple-output combinational logic network with  $n$  input line and  $2^N$  output line.



3

  
# Decoder

$$\begin{aligned}
 m_0 &= \bar{B}\bar{A} \\
 m_1 &= \bar{B}A \\
 m_2 &= B\bar{A} \\
 m_3 &= BA
 \end{aligned}$$



4

# Decoder

 

5

# Decoder



Let us implement the following logic functions using decoders and logic gates.

$$f(Q, X, P) = \sum m(0, 1, 4, 6, 7)$$

$$= \prod M(2, 3, 5)$$

We may implement the function in several ways:

  
1. Use a decoder (with active-high outputs) with an OR gate:  
 $f(Q, X, P) = m_0 + m_1 + m_4 + m_6 + m_7$
2. Use a decoder (with active-low outputs) with a NAND gate:  
 $f(Q, X, P) = \overline{m_2 \cdot m_3 \cdot m_5}$
3. Use a decoder (with active-high outputs) with a NOR gate:  
 $f(Q, X, P) = \overline{m_2 + m_3 + m_5}$
4. Use a decoder (with active-low outputs) with an AND gate:  
 $f(Q, X, P) = \overline{m_2} \cdot \overline{m_3} \cdot \overline{m_5}$



6



# Decoder

- Enable Control Input

 

7

# Decoder

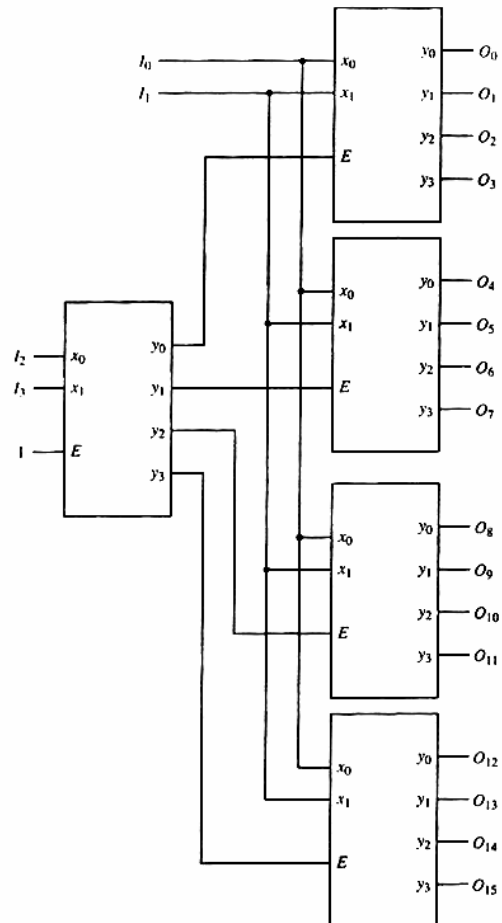 

8



# Decoder

- Standard MSI Decoder

'S138 'LS138


ENABLE		SELECT			OUTPUTS							
G <sub>1</sub>	G <sub>2</sub> <sup>*</sup>	C	B	A	Y <sub>0</sub>	Y <sub>1</sub>	Y <sub>2</sub>	Y <sub>3</sub>	Y <sub>4</sub>	Y <sub>5</sub>	Y <sub>6</sub>	Y <sub>7</sub>
X	H	X	X	X	H	H	H	H	H	H	H	H
L	X	X	X	X	H	H	H	H	H	H	H	H
H	L	L	L	L	L	X	H	H	H	H	H	H
H	L	L	L	H	H	L	H	H	H	H	H	H
H	L	L	H	L	H	H	L	H	H	H	H	H
H	L	L	H	H	H	H	H	L	H	H	H	H
H	L	H	L	L	H	H	H	H	L	H	H	H
H	L	H	H	L	H	H	H	H	H	L	H	H
H	L	H	H	H	H	H	H	H	H	H	L	H

  \* G<sub>2</sub> = G<sub>2A</sub> + G<sub>2B</sub>



9


# Decoder

 

'S139 'LS139

(EACH DECODER / DEMULTIPLEXER)


INPUTS		SELECT		OUTPUTS			
ENABLE	G	B	A	Y <sub>0</sub>	Y <sub>1</sub>	Y <sub>2</sub>	Y <sub>3</sub>
H	X	X	X	H	H	H	H
L	L	L	L	L	H	H	H
L	L	L	H	H	L	H	H
L	L	H	L	H	H	L	H
L	L	H	H	H	H	H	L

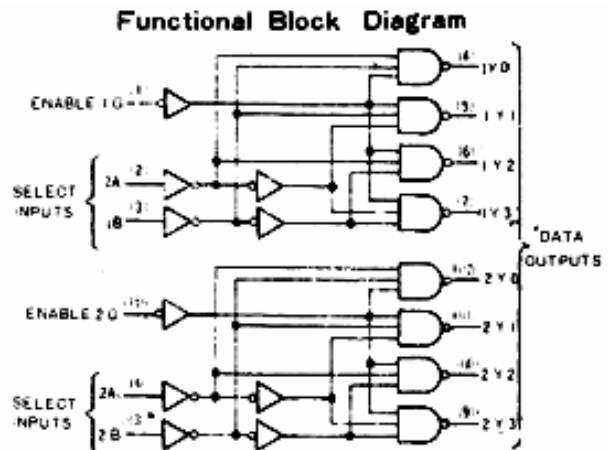


10

# Decoder

- Standard MSI Decoder

 


Inputs					Outputs																	
$\overline{G1}$	$\overline{G2}$	D	C	B	A	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	
L	L	L	L	L	L	L	H	H	H	H	H	H	H	H	H	H	H	H	H	H	H	H
L	L	L	L	L	H	H	L	H	H	H	H	H	H	H	H	H	H	H	H	H	H	H
L	L	L	L	H	L	H	H	L	H	H	H	H	H	H	H	H	H	H	H	H	H	H
L	L	L	H	L	L	H	H	H	L	H	H	H	H	H	H	H	H	H	H	H	H	H
L	L	L	H	L	H	H	H	H	H	L	H	H	H	H	H	H	H	H	H	H	H	H
L	L	L	H	H	L	H	H	H	H	H	L	H	H	H	H	H	H	H	H	H	H	H
L	L	L	H	H	L	H	H	H	H	H	H	L	H	H	H	H	H	H	H	H	H	H
L	L	L	H	H	H	H	H	H	H	H	H	H	L	H	H	H	H	H	H	H	H	H
L	L	H	L	L	L	H	H	H	H	H	H	H	H	H	L	H	H	H	H	H	H	H
L	L	H	L	L	H	H	H	H	H	H	H	H	H	H	H	L	H	H	H	H	H	H
L	L	H	L	H	L	H	H	H	H	H	H	H	H	H	H	H	L	H	H	H	H	H
L	L	H	H	L	L	H	H	H	H	H	H	H	H	H	H	H	H	L	H	H	H	H
L	L	H	H	L	H	H	H	H	H	H	H	H	H	H	H	H	H	H	L	H	H	H
L	L	H	H	H	L	H	H	H	H	H	H	H	H	H	H	H	H	H	H	L	H	H
L	L	H	H	H	H	H	H	H	H	H	H	H	H	H	H	H	H	H	H	H	L	H
H	L	x	x	x	x	H	H	H	H	H	H	H	H	H	H	H	H	H	H	H	H	H
L	H	x	x	x	x	H	H	H	H	H	H	H	H	H	H	H	H	H	H	H	H	H
H	H	x	x	x	x	H	H	H	H	H	H	H	H	H	H	H	H	H	H	H	H	H

 
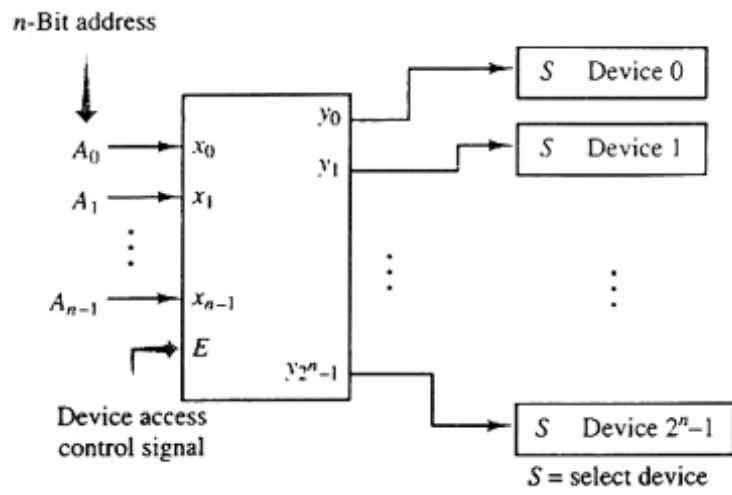
# Decoder

- Decoder Application
  - Address Decoding



# Decoder

## ■ Minterm Generation

Realize the following functions using a 74154 and logic gates:

$$f_1(W, X, Y, Z) = \sum m(1, 9, 12, 15)$$

$$f_2(W, X, Y, Z) = \sum m(0, 1, 2, 3, 4, 5, 7, 8, 10, 11, 12, 13, 14, 15)$$

Using implementations 2 and 3 from Example 4.1:

$$f_1(W, X, Y, Z) = \overline{m}_1 \overline{m}_9 \overline{m}_{12} \overline{m}_{15}$$


and

$$f_2(W, X, Y, Z) = \overline{m}_6 \cdot \overline{m}_9$$

13

# Decoder

## ■ Minterm Generation

 

14


# Encoder

- Encoder is a combinational logic module that assigns a unique output code.
- Each input signal applied to the device.

Design an encoder for four input lines if one and only one is active at any moment in time. See Fig. 4.17a.

Let us define the code:

	$A_1$	$A_0$
$X_0 \rightarrow$	0	0
$X_1 \rightarrow$	0	1
$X_2 \rightarrow$	1	0
$X_3 \rightarrow$	1	1

 

15

# Encoder

$X_3$	$X_2$	$X_1$	$X_0$	$A_1$	$A_0$
0	0	0	0	<i>d</i>	<i>d</i>
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	<i>d</i>	<i>d</i>
0	1	0	0	1	0
0	1	0	1	<i>d</i>	<i>d</i>
0	1	1	0	<i>d</i>	<i>d</i>
0	1	1	1	<i>d</i>	<i>d</i>
1	0	0	0	1	1
1	0	0	1	<i>d</i>	<i>d</i>
1	0	1	0	<i>d</i>	<i>d</i>
1	0	1	1	<i>d</i>	<i>d</i>
1	1	0	0	<i>d</i>	<i>d</i>
1	1	0	1	<i>d</i>	<i>d</i>
1	1	1	0	<i>d</i>	<i>d</i>
1	1	1	1	<i>d</i>	<i>d</i>

$$A_1 = X_3 + X_2$$

$$A_0 = X_3 + X_1$$

16




# Encoder

Design a four-line encoder that outputs a zero code unless one and only one input line is active.

Let us define the code:




	$A_2$	$A_1$	$A_0$
$X_1 \rightarrow$	0	0	1
$X_2 \rightarrow$	0	1	0
$X_3 \rightarrow$	0	1	1
$X_4 \rightarrow$	1	0	0
All others $\rightarrow$	0	0	0

 

17

# Encoder

$X_4$	$X_3$	$X_2$	$X_1$	$A_2$	$A_1$	$A_0$
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	0	0
0	1	0	0	0	1	1
0	1	0	1	0	0	0
0	1	1	0	0	0	0
0	1	1	1	0	0	0
1	0	0	0	1	0	0
1	0	0	1	0	0	0
1	0	1	0	0	0	0
1	0	1	1	0	0	0
1	1	0	0	0	0	0
1	1	0	1	0	0	0
1	1	1	0	0	0	0
1	1	1	1	0	0	0

   

$$A_2 = X_4 \bar{X}_3 \bar{X}_2 \bar{X}_1$$

$$A_1 = \bar{X}_4 \bar{X}_3 X_2 \bar{X}_1 + \bar{X}_4 X_3 \bar{X}_2 \bar{X}_1$$


$$A_0 = \bar{X}_4 \bar{X}_3 \bar{X}_2 X_1 + \bar{X}_4 X_3 \bar{X}_2 \bar{X}_1$$

18

# Encoder

## Priority Encoder



	$A_1$	$A_0$
$X_0 \rightarrow$	0	0
$X_1 \rightarrow$	0	1
$X_2 \rightarrow$	1	0
$X_3 \rightarrow$	1	1

 

Inputs				Outputs			
$X_3$	$X_2$	$X_1$	$X_0$	$A_1$	$A_0$	$GS$	$EO$
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	1	1	0
0	0	1	1	0	1	1	0
0	1	0	0	1	0	1	0
0	1	0	1	1	0	1	0
0	1	1	0	1	0	1	0
0	1	1	1	1	0	1	0
1	0	0	0	1	1	1	0
1	0	0	1	1	1	1	0
1	0	1	0	1	1	1	0
1	0	1	1	1	1	1	0
1	1	0	0	1	1	1	0
1	1	0	1	1	1	1	0
1	1	1	0	1	1	1	0
1	1	1	1	1	1	1	0

19

# Encoder

  

$$A_1 = X_2 + X_3$$

$$A_0 = X_3 + X_1\bar{X}_2$$

$$EO = \overline{GS} = \overline{X_3 + X_2 + X_1 + X_0}$$

20



# Encoder

- Standard MSI Encoder


**'147**

INPUTS									OUTPUTS			
1	2	3	4	5	6	7	8	9	D	C	B	A
H	H	H	H	H	H	H	H	H	H	H	H	H
X	X	X	X	X	X	X	X	L	L	H	H	L
X	X	X	X	X	X	X	L	H	L	H	H	H
X	X	X	X	X	L	H	H	H	H	L	L	L
X	X	X	X	L	H	H	H	H	H	L	H	L
X	X	L	H	H	H	H	H	H	H	H	L	L
X	L	H	H	H	H	H	H	H	H	H	L	H
L	H	H	H	H	H	H	H	H	H	H	H	L

Pin Assignment (Top View)

  


# Encoder

 

**'148**



EI	INPUTS							OUTPUTS					
	0	1	2	3	4	5	6	7	A2	A1	A0	GS	EO
H	X	X	X	X	X	X	X	X	H	H	H	H	H
L	H	H	H	H	H	H	H	H	H	H	H	H	L
L	X	X	X	X	X	X	L	L	L	L	L	L	H
L	X	X	X	X	X	L	H	L	H	L	L	H	H
L	X	X	X	L	H	H	H	L	H	H	L	H	H
L	X	X	L	H	H	H	H	H	L	L	L	H	H
L	X	L	H	H	H	H	H	H	H	L	L	H	H
L	L	H	H	H	H	H	H	H	H	H	L	H	H

 

148 8-LINE-TO-3-LINE PRIORITY ENCODER

  
# Multiplexers / Data Selectors

- Multiplexer is a modular device that selects one of many input lines to appear on a single output line.



23


# Multiplexers / Data Selectors

 


B	A	Y
0	0	$D_0$
0	1	$D_1$
1	0	$D_2$
1	1	$D_3$

$$Y = (\bar{B}\bar{A})D_0 + (\bar{B}A)D_1 + (B\bar{A})D_2 + (BA)D_3$$

$$Y = \sum_{i=0}^3 m_i D_i$$

 


(c)

 

(d)

24


# Multiplexers / Data Selectors

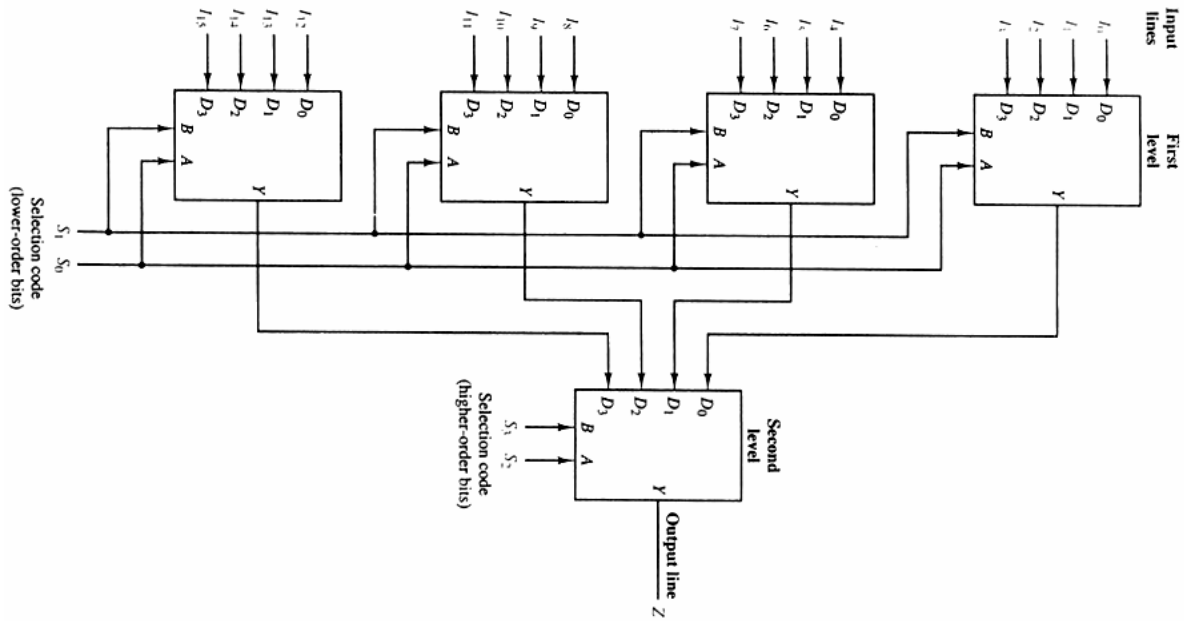

25


# Multiplexers / Data Selectors

- Standard MSI Multiplexers

 


74151A, 74LS151, 74S151

INPUTS			STROBE S	OUTPUTS	
C	B	A		Y	W
X	X	X	H	L	H
L	L	L	L	D0	D0
L	L	H	L	D1	D1
L	H	L	L	D2	D2
L	H	H	L	D3	D3
H	L	L	L	D4	D4
H	L	H	L	D5	D5
H	H	L	L	D6	D6
H	H	H	L	D7	D7

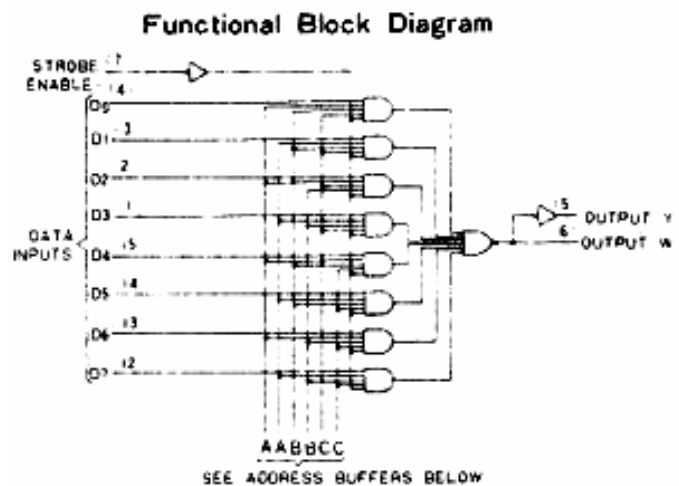


26

# Multiplexers / Data Selectors

 


**'150**

INPUTS				STROBE	OUTPUT
D	C	B	A	S	W
X	X	X	X	H	H
L	L	L	L	L	E0
L	L	L	H	L	E1
L	L	H	L	L	E2
L	L	H	H	L	E3
L	H	L	L	L	E4
L	H	L	H	L	E5
L	H	H	L	L	E6
L	H	H	H	L	E7
H	L	L	L	L	E8
H	L	L	H	L	E9
H	L	H	L	L	E10
H	L	H	H	L	E11
H	H	L	L	L	E12
H	H	L	H	L	E13
H	H	H	L	L	E14
H	H	H	H	L	E15

 


# Multiplexers / Data Selectors

 


'153, 'S153, 'LS153, 'L153

SELECT INPUTS		DATA INPUTS				STROBE	OUTPUT
B	A	C0	C1	C2	C3	G	Y
X	X	X	X	X	X	H	L
L	L	L	X	X	X	L	L
L	L	H	X	X	X	L	H
L	H	X	L	X	X	L	L
L	H	X	H	X	X	L	H
H	L	X	X	L	X	L	L
H	L	X	X	H	X	L	H
H	H	X	X	X	L	L	L
H	H	X	X	X	H	L	H

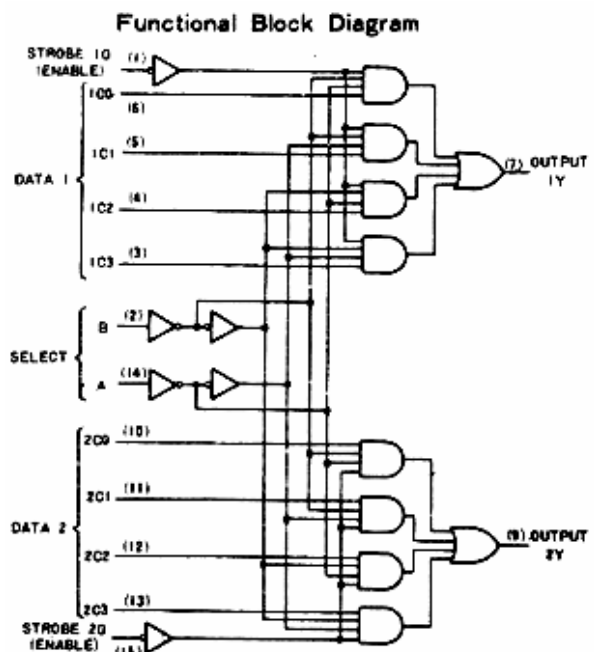

# Multiplexers / Data Selectors

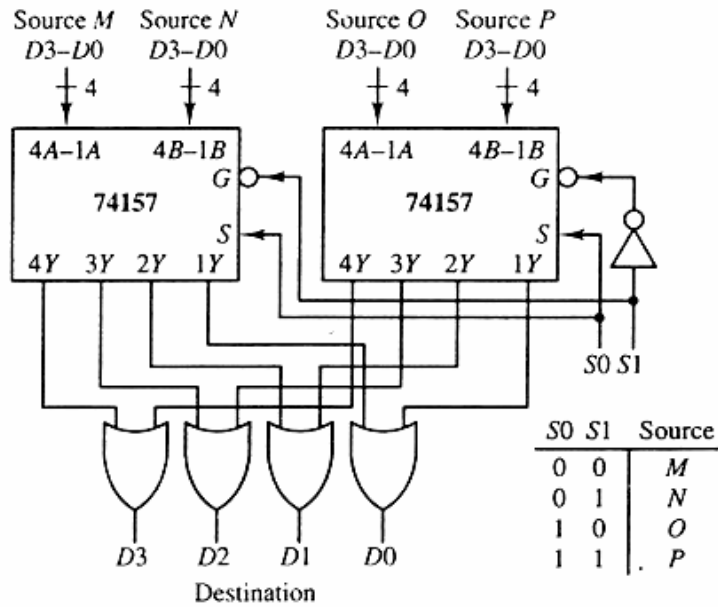

29


# Multiplexers / Data Selectors

## Application of Multiplexers

Use a 74151A to implement  
 $f(x_1, x_2, x_3) = \sum m(0, 2, 3, 5)$ .

$i$	C	B	A	$Y$
	$x_1$	$x_2$	$x_3$	$f$
0	0	0	0	1 $D_0=1$
1	0	0	1	0 $D_1=0$
2	0	1	0	1 $D_2=1$
3	0	1	1	1 $D_3=1$
4	1	0	0	0 $D_4=0$
5	1	0	1	1 $D_5=1$
6	1	1	0	0 $D_6=0$
7	1	1	1	0 $D_7=0$

(a)

 

30

# Multiplexers / Data Selectors


Implement  $f(a,b,c) = ab + \bar{b}c$  using the 4-to-1 multiplexer of Fig. 4.23.

$$f(a,b,c) = ab + \bar{b}c$$

$$= ab\bar{c} + abc + \bar{a}\bar{b}c + a\bar{b}c$$

$$f(a,b,c) = \bar{a}\bar{b}(c) + a\bar{b}(c) + ab(\bar{c} + c)$$


a	b	$f(a,b,c)$	MUX Inputs
0	0	c	$D_0 = c$
0	1	0	$D_1 = 0$
1	0	c	$D_2 = c$
1	1	1	$D_3 = 1$

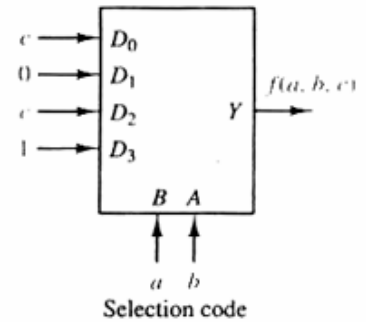

(a)

b	c	$f(a,b,c)$	MUX Inputs
0	0	0	$D_0 = 0$
0	1	1	$D_1 = 1$
1	0	a	$D_2 = a$
1	1	a	$D_3 = a$

(c)

 

# Multiplexers / Data Selectors

Implement

$f(X_1, X_2, X_3, X_4) = \sum m(0, 1, 2, 3, 4, 9, 13, 14, 15)$  using a 74151A.


0 } logic 0

1 } logic 1

0 } variable  $X_4$

1 } variable  $\bar{X}_4$


	C	B	A				Y
i	$X_1$	$X_2$	$X_3$	$X_4$	f	f	
0	0	0	0	0	1		$D_0 = 1$
1	0	0	1	0	1	1	$D_1 = 1$
2	0	1	0	0	1	$\bar{X}_4$	$D_2 = \bar{X}_4$
3	0	1	1	0	0	0	$D_3 = 0$
4	1	0	0	0	0		
	1	0	0	1	1	$X_4$	$D_4 = X_4$
5	1	0	1	0	0	0	$D_5 = 0$
	1	0	1	1	0	0	
6	1	1	0	0	0		
	1	1	0	1	1	$X_4$	$D_6 = X_4$
7	1	1	1	0	1	1	
	1	1	1	1	1	1	$D_7 = 1$

 





# Demultiplexers / Data Distributors

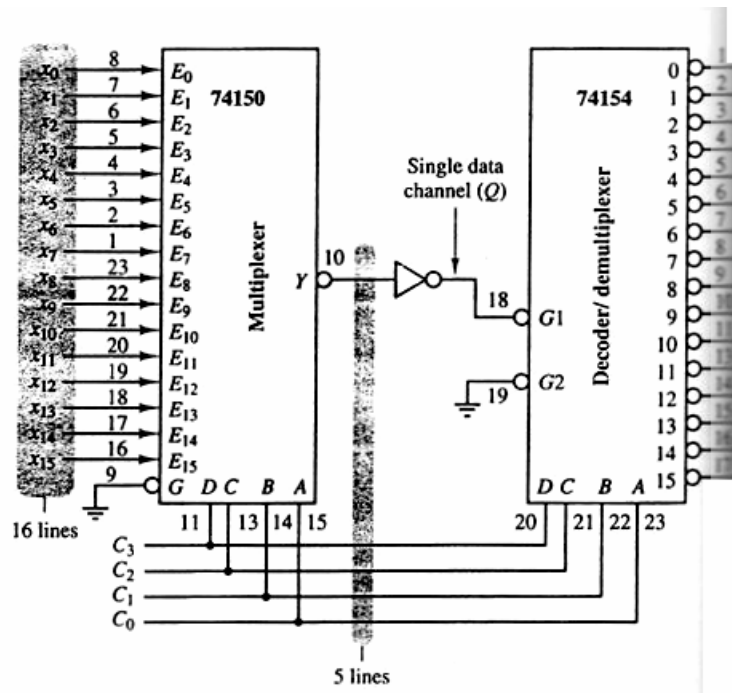

35

36