



# Binary Arithmetic Element

---

1



## Agenda

---

- Basic Binary Adder Circuit
- Binary Adder Module
- High Speed Adder Module
- Binary Subtraction Circuit
- Arithmetic Overflow Detection
- Computer Arithmetic Unit


2

# Basic Binary Adder Circuit

## ■ Half Adder

$$s_i = x_i \oplus y_i$$

$$c_i = x_i y_i$$

 

$x_i$	$y_i$	$c_i$	$s_i$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

(b)


3

# Basic Binary Adder Circuit
 
## ■ Full Adder

$$s_i = x_i \oplus y_i \oplus c_{i-1}$$

$$c_i = x_i y_i + x_i c_{i-1} + y_i c_{i-1}$$




$x_i$	$y_i$	$c_{i-1}$	$c_i$	$s_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

(e)

4
 
# Basic Binary Adder Circuit

- Pseudo Parallel Adder
  - Employs n-1 Full-adder and 1 Half-adder




the two input data words. The operation to be performed is

$$\begin{array}{r}
 X \\
 + Y \\
 \hline
 Z
 \end{array}
 \quad
 \begin{array}{r}
 (x_{n-1}x_{n-2} \dots x_1x_0)_2 \\
 + (y_{n-1}y_{n-2} \dots y_1y_0)_2 \\
 \hline
 (z_nz_{n-1}z_{n-2} \dots z_1z_0)_2
 \end{array}$$

# Binary Adder Module

- 7482 Two-bit Adder

Inputs				Outputs					
A2	A1	B2	B1	When C0 = L			When C0 = H		
				C2	Σ2	Σ1	C2	Σ2	Σ1
L	L	L	L	L	L	L	L	L	H
L	L	L	H	L	L	H	L	H	L
L	L	H	L	L	H	L	L	H	H
L	L	H	H	L	H	H	H	L	L
L	H	L	L	L	L	H	L	H	L
L	H	L	H	L	H	L	L	H	H
L	H	H	L	L	H	H	H	L	L
L	H	H	H	H	L	L	H	L	H
H	L	L	L	L	H	L	L	H	H
H	L	L	H	L	H	H	H	L	L
H	L	H	L	H	L	L	H	L	H
H	L	H	H	H	L	H	H	H	L
H	H	L	L	L	H	H	H	L	L
H	H	L	H	H	L	L	H	L	H
H	H	H	L	H	L	H	H	H	L
H	H	H	H	H	H	L	H	H	H

 

# Binary Adder Module

$$\begin{aligned}
 C_1 &= C_0 \cdot A_1 + C_0 \cdot B_1 + A_1 \cdot B_1 \\
 \Sigma_1 &= C_0 \cdot \bar{C}_1 + A_1 \cdot \bar{C}_1 + B_1 \cdot \bar{C}_1 + A_1 \cdot B_1 \cdot C_0 \\
 &= \bar{C}_1(C_0 + A_1 + B_1) + A_1 \cdot B_1 \cdot C_0 \\
 &= (\bar{C}_0 + \bar{A}_1)(\bar{C}_0 + \bar{B}_1)(\bar{A}_1 + \bar{B}_1)(C_0 + A_1 + B_1) + A_1 \cdot B_1 \cdot C_0 \\
 &= (\bar{C}_0 + \bar{A}_1 \cdot \bar{B}_1)(\bar{A}_1 + \bar{B}_1)(C_0 + A_1 + B_1) + A_1 \cdot B_1 \cdot C_0 \\
 &= [\bar{C}_0(A_1 + B_1) + C_0 \cdot \bar{A}_1 \cdot \bar{B}_1](\bar{A}_1 + \bar{B}_1) + A_1 \cdot B_1 \cdot C_0 \\
 &= \bar{C}_0 \cdot \bar{A}_1 \cdot B_1 + \bar{C}_0 \cdot A_1 \cdot \bar{B}_1 + C_0 \cdot \bar{A}_1 \cdot \bar{B}_1 + A_1 \cdot B_1 \cdot C_0 \\
 &= C_0 \oplus A_1 \oplus B_1
 \end{aligned}$$

$$\begin{aligned}
 C_2 &= C_1 \cdot A_2 + C_1 \cdot B_2 + A_2 \cdot B_2 \\
 \Sigma_2 &= C_1 \oplus A_2 \oplus B_2
 \end{aligned}$$

The 7482 pseudo-parallel adder module.

7

# Binary Adder Module

## 7483 4-Bits Adder Module


$$\begin{aligned}
 P_i &= \overline{(B_i \cdot A_i)}(A_i + B_i) \\
 &= (\bar{A}_i + \bar{B}_i)(A_i + B_i) \\
 &= A_i \oplus B_i \\
 \Sigma_i &= P_i \oplus C_{i-1} \\
 &= A_i \oplus B_i \oplus C_{i-1}
 \end{aligned}$$

and

$$\begin{aligned}
 C_1 &= \overline{\overline{(\bar{C}_0 \cdot \bar{A}_1 \cdot \bar{B}_1)} + (\bar{A}_1 + \bar{B}_1)} \\
 &= \overline{(\bar{C}_0 \cdot \bar{A}_1 \cdot \bar{B}_1)} \cdot (\bar{A}_1 + \bar{B}_1) \\
 &= (C_0 + (A_1 \cdot B_1)) \cdot (A_1 + B_1) \\
 &= C_0 \cdot A_1 + C_0 \cdot B_1 + A_1 \cdot B_1
 \end{aligned}$$

In a similar manner, we may find
 
$$C_i = C_{i-1} \cdot A_i + C_{i-1} \cdot B_i + A_i \cdot B_i$$



8

# High Speed Adder

- Fully Parallel Adder

$$c_0 = x_0 y_0$$

$$c_1 = x_1 y_1 \bar{c}_0 + x_1 y_1 c_0 + x_1 \bar{y}_1 c_0 + \bar{x}_1 y_1 c_0$$

$$= x_1 y_1 + (x_1 \oplus y_1) c_0$$

$$= x_1 y_1 + (x_1 \oplus y_1)(x_0 y_0)$$

$$c_2 = x_2 y_2 + (x_2 \oplus y_2) c_1$$

$$= x_2 y_2 + (x_2 \oplus y_2)[x_1 y_1 + (x_1 \oplus y_1)(x_0 y_0)]$$

$$= x_2 y_2 + (x_2 \oplus y_2)(x_1 y_1) + (x_2 \oplus y_2)(x_1 \oplus y_1)(x_0 y_0)$$

9

# High Speed Adder

- Carry Look-Ahead Adder




$$c_0 = g_0$$

$$c_1 = g_1 + p_1 c_0$$

$$= g_1 + p_1 g_0$$

$$c_2 = g_2 + p_2 c_1$$


$$= g_2 + p_2 g_1 + p_2 p_1 g_0$$

  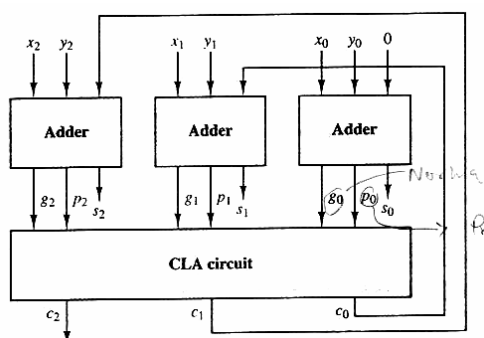

10
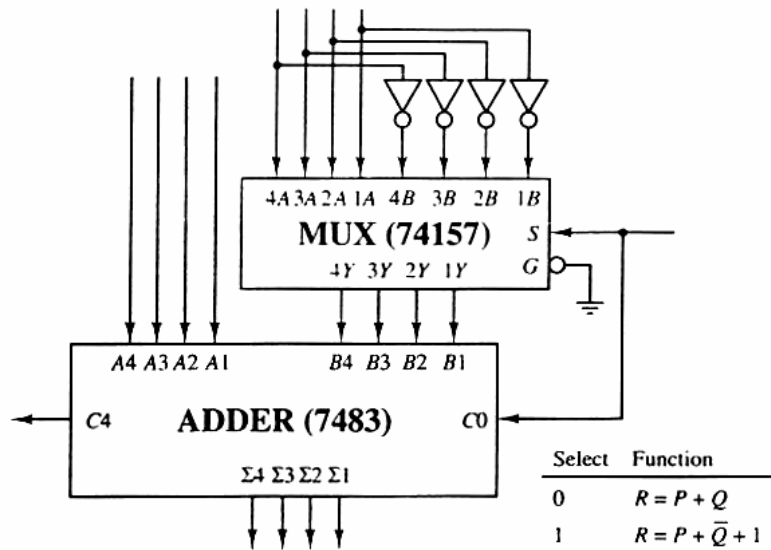
# Binary Subtraction Circuit

$$\begin{aligned}
 (R)_2 &= (P)_2 - (Q)_2 \\
 &= (P)_2 + (-Q)_2 \\
 &= (P)_2 + [\bar{Q}]_2 \\
 &= (P)_2 + (\bar{Q})_2 + 1
 \end{aligned}$$



11


# Arithmetic Overflow Detection

$$-2^{n-1} \leq N \leq 2^{n-1} - 1$$

Adder Inputs			Adder Outputs		Overflow
$a_{n-1}$	$b_{n-1}$	$c_{n-2}$	$c_{n-1}$	$s_{n-1}$	V
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	1	1	0


12

# Arithmetic Overflow Detection

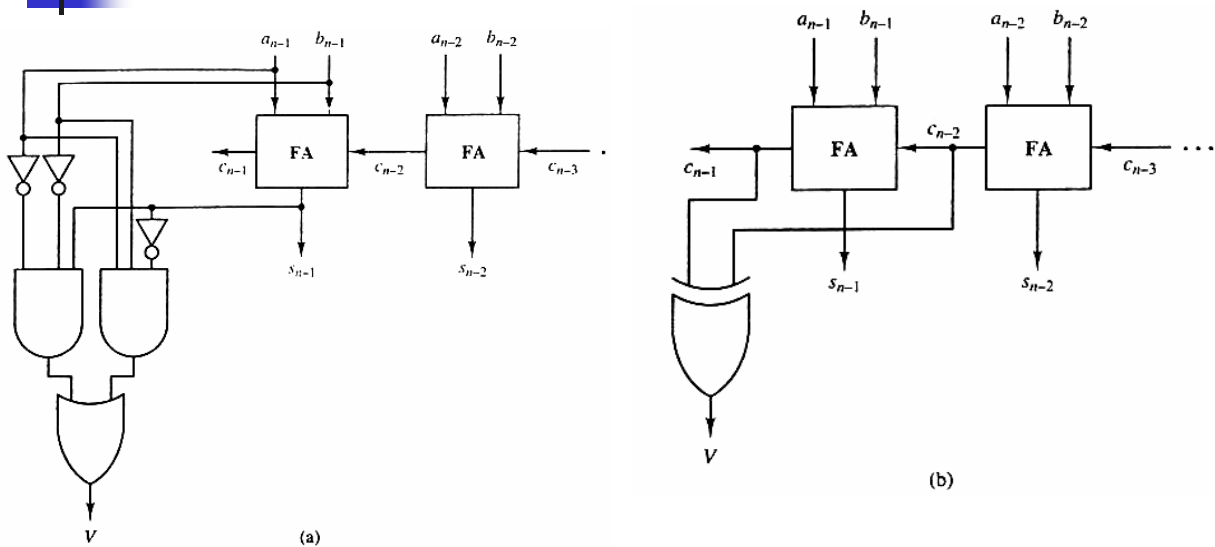


**Figure 4.42** Two's complement overflow detection. (a) Using sign bits. (b) Using carry bits.

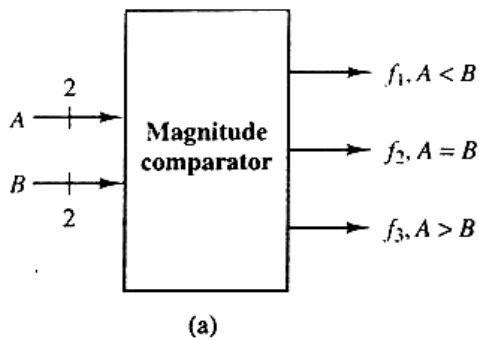 **Design a comparator that will compare the two words  $A = (A_1A_0)_2$  and  $B = (B_1B_0)_2$  in binary code.**



$i$	$A_1$	$A_0$	$B_1$	$B_0$	$f_1$	$f_2$	$f_3$
0	0	0	0	0	0	1	0
1	0	0	0	1	1	0	0
2	0	0	1	0	1	0	0
3	0	0	1	1	1	0	0
4	0	1	0	0	0	0	1
5	0	1	0	1	0	1	0
6	0	1	1	0	1	0	0
7	0	1	1	1	1	0	0
8	1	0	0	0	0	0	1
9	1	0	0	1	0	0	1
10	1	0	1	0	0	1	0
11	1	0	1	1	1	0	0
12	1	1	0	0	0	0	1
13	1	1	0	1	0	0	1
14	1	1	1	0	0	0	1
15	1	1	1	1	0	1	0



$$f_1 = \bar{A}_1 B_1 + \bar{A}_1 \bar{A}_0 B_0 + \bar{A}_0 B_1 B_0$$

$$f_2 = \bar{A}_1 \bar{A}_0 \bar{B}_1 \bar{B}_0 + \bar{A}_1 A_0 \bar{B}_1 B_0 + A_1 \bar{A}_0 B_1 \bar{B}_0 + A_1 A_0 B_1 B_0$$


$$f_3 = A_1 \bar{B}_1 + A_0 \bar{B}_1 \bar{B}_0 + A_1 A_0 \bar{B}_0$$

Use the 7485 to construct a 16-bit magnitude comparator.

Comparing inputs				Cascading inputs			Outputs		
A3, B3	A2, B2	A1, B1	A0, B0	A > B	A < B	A = B	A > B	A < B	A = B
A3 > B3	x	x	x	x	x	x	H	L	L
A3 < B3	x	x	x	x	x	x	L	H	L
A3 = B3	A2 > B2	x	x	x	x	x	H	L	L
A3 = B3	A2 < B2	x	x	x	x	x	L	H	L
A3 = B3	A2 = B2	A1 > B1	x	x	x	x	H	L	L
A3 = B3	A2 = B2	A1 < B1	x	x	x	x	L	H	L
A3 = B3	A2 = B2	A1 = B1	A0 > B0	x	x	x	H	L	L
A3 = B3	A2 = B2	A1 = B1	A0 < B0	x	x	x	L	H	L
A3 = B3	A2 = B2	A1 = B1	A0 = B0	H	L	L	H	L	L
A3 = B3	A2 = B2	A1 = B1	A0 = B0	L	H	L	L	H	L
A3 = B3	A2 = B2	A1 = B1	A0 = B0	L	L	H	L	L	H
A3 = B3	A2 = B2	A1 = B1	A0 = B0	H	H	L	L	L	L
A3 = B3	A2 = B2	A1 = B1	A0 = B0	L	L	L	H	H	L

(b)



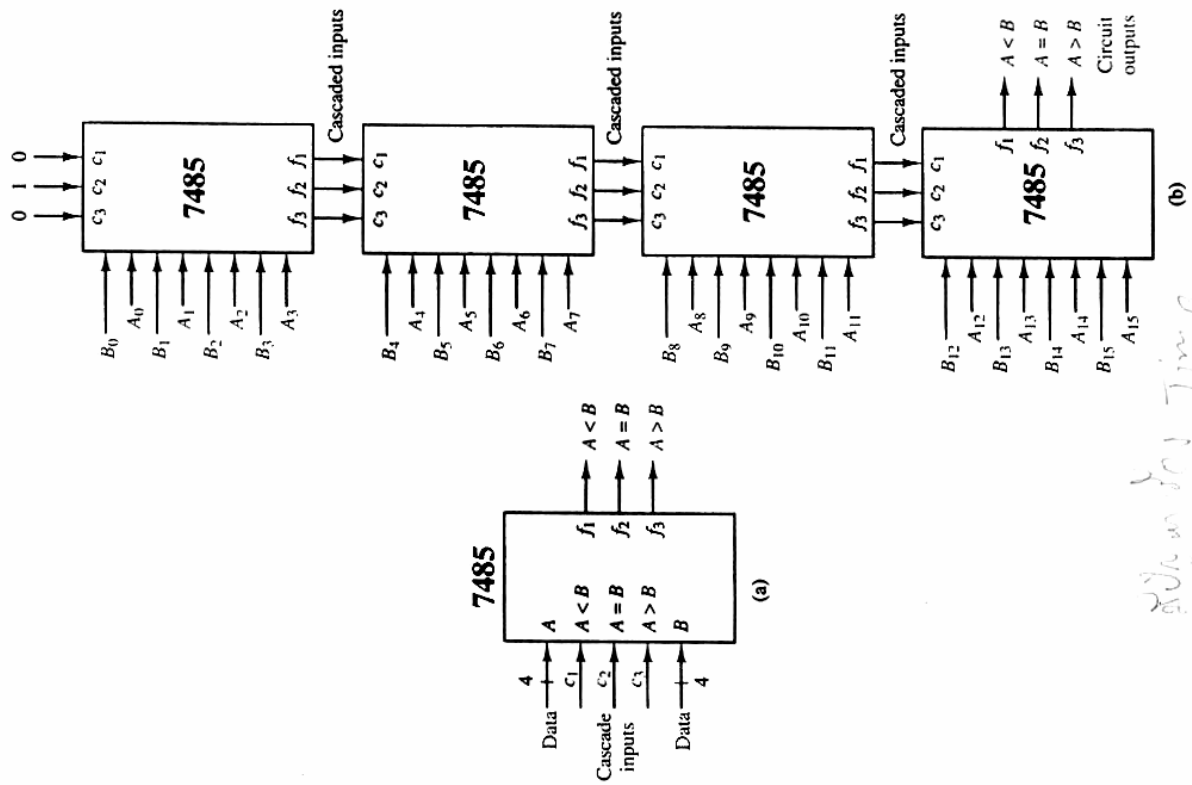

# A Computer Arithmetic Unit


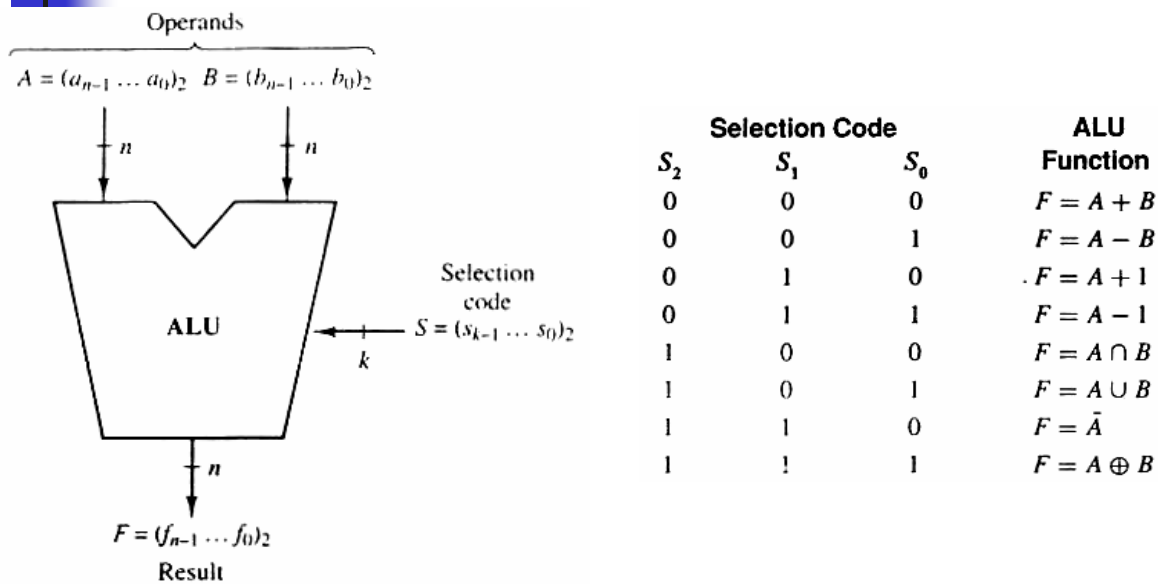


Figure 4.47 ALU logic symbol.

# A Computer Arithmetic Unit

 

19

# A Computer Arithmetic Unit


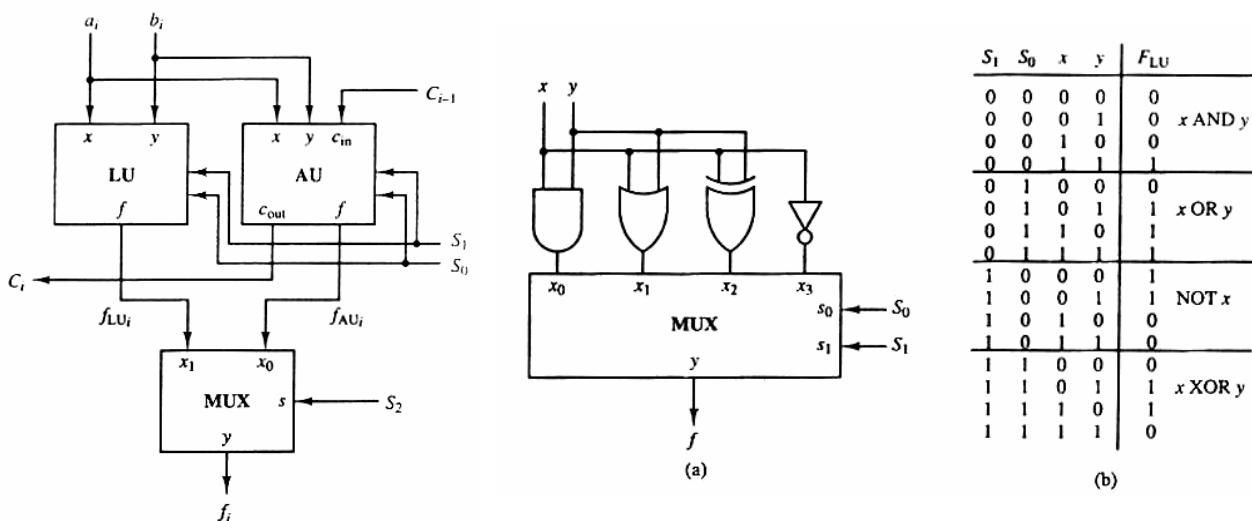



Figure 4.49 One-bit ALU partitioned into separate arithmetic and logic units.

20

# A Computer Arithmetic Unit

 

(c)

 

(d)

21

# A Computer Arithmetic Unit

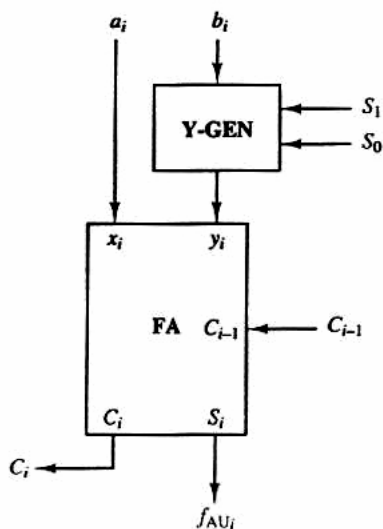


TABLE 4.6 VALUES OF  $y_i$  AND  $C_{-1}$  FOR THE ARITHMETIC FUNCTIONS

Function	$S_1$	$S_0$	$y_i$	$C_{-1}$
Add	0	0	$b_i$	0
Subtract	0	1	$\bar{b}_i$	1
Increment	1	0	0	1
Decrement	1	1	1	0

22

# A Computer Arithmetic Unit

$S_1$	$S_0$	$b_i$	$y_i$	
0	0	0	0	Add
0	0	1	1	
0	1	0	1	Subtract
0	1	1	0	
1	0	0	0	Increment
1	0	1	0	
1	1	0	1	Decrement
1	1	1	1	

(a)

$S_1 S_0$		$b_i$			
		00	01	11	10
0	0	0	1	1	0
	1	1	0	1	0
1	0	1	0	1	0
	1	1	0	1	0

(b)

$S_1$	$S_0$	$C_{-1}$	
0	0	0	Add
0	1	1	Subtract
1	0	1	Increment
1	1	0	Decrement

(a)

$S_1 S_0$		$C_{-1}$	
		0	1
0	0	0	1
	1	1	0
1	0	1	0
	1	0	1

(b)