

# Introduction to Sequential Devices

---

1



## Agenda


---

- Models for Sequential Circuit
- Memory Devices
- Latches
- Flip-flops

2

# Models for Sequential Devices
 
## ■ Block Diagram Representation


 


**Figure 6.1** The sequential circuit model. (a) Combinational logic circuit. (b) Sequential logic circuit.

3

# Models for Sequential Devices

## ■ State Tables and Diagram

 

4

# Models for Sequential Devices

- 1 input variable  $x$ , 2 state variable  $y_1$  and  $y_2$ , and 1 output variable  $z$ .

Inputs:  $x = 0$   
 $x = 1$

States:  $[y_1, y_2] = [00] \equiv A$   
 $[y_1, y_2] = [01] \equiv B$   
 $[y_1, y_2] = [10] \equiv C$   
 $[y_1, y_2] = [11] \equiv D$

Outputs:  $z = 0$   
 $z = 1$

5

# Models for Sequential Devices

$x = 0110101100$


The circuit will behave as follows when the initial state is A:

Time:	0	1	2	3	4	5	6	7
Present state:	A	D	B	A	D	B	B	A
Input:	0	1	1	0	1	0	1	1
Next state:	D	B	A	D	B	B	A	C
Output:	0	1	0	0	1	1	0	1

Hence, this input sequence applied to the machine in state A sequence

$z = 0100110111$

Present state	Input $x$	
	0	1
A	D/0	C/1
B	B/1	A/0
C	C/1	D/0
D	A/0	B/1

 



6

## Memory Devices

- The two element types most commonly used in switching circuits are *latch* and *flip-flop*.
- Latch is a memory element whose excitation input signals control the state of the devices.
- Flip-flop differs from a latch in that it has control signal called a *clock*.

7

## Memory Devices

  


a) Latch responds immediately to excitation.

b) Flip-flop responds only on a clock signal.

8

# Latch



## ■ Set-Reset Latch

 

**Figure 6.5** Set latch. (a) OR gate. (b) Feedback added. (c) Output set to 1. (d) Feedback holds  $Q = 1$ .





9

# Latch

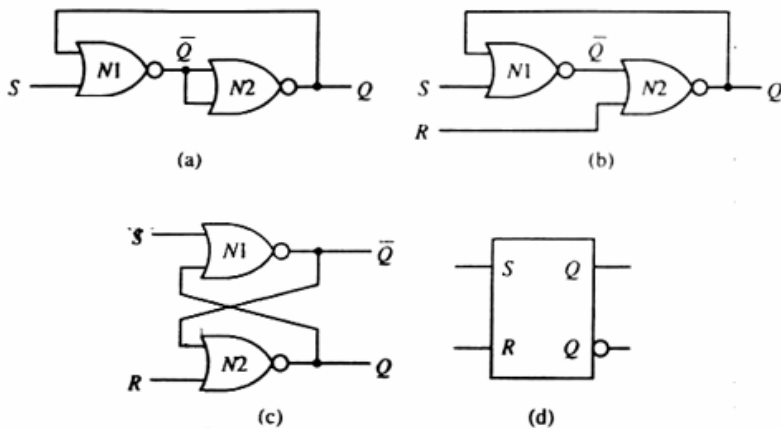 

10

# Latch

    



# Latch

- SR Latch Excitation table

Excitation inputs		Present state	Next state	
S	R	Q	Q*	
0	0	0	0	No change
0	0	1	1	
0	1	0	0	Reset
0	1	1	0	
1	0	0	1	Set
1	0	1	1	
1	1	0	x	Not allowed
1	1	1	x	

(a)


$$Q^* = S + \bar{R}Q$$

  

# Latch
 
## Gate SR Latch

- A control signal,  $C$ , is added to an SR latch to apply the inputs  $S$  and  $R$ .




13

# Latch

Enable inputs	Excitation inputs		Present state	Next state	
	$C$	$S$			
0	x	x	0	0	Hold
0	x	x	1	1	
1	0	0	0	0	No change
1	0	0	1	1	
1	0	1	0	0	Reset
1	0	1	1	0	
1	1	0	0	1	Set
1	1	0	1	1	
1	1	1	0	x	Not allowed
1	1	1	1	x	

(a)

$$Q^* = SC + \bar{R}Q + \bar{C}Q$$

 


(b)

Figure 6.14 Gated SR latch characteristics. (a) Excitation table. (b) State diagram.


14

# Latch

## Delay Latch

 

Enable input <i>C</i>	Excitation input <i>D</i>	Present state <i>Q</i>	Next state <i>Q*</i>
0	x	0	0 Hold
0	x	1	1 Hold
1	0	0	0 Store 0
1	0	1	0 Store 1
1	1	0	1 Store 1
1	1	1	1 Store 1



 


$$\begin{aligned}
 Q^* &= SC + \bar{R}Q + \bar{C}Q \\
 &= DC + (\bar{D})Q + \bar{C}Q \\
 &= DC + DQ + \bar{C}Q \\
 &= DC + \bar{C}Q
 \end{aligned}$$

15

# Flip-flop

## Master-Slave SR Flip-flop

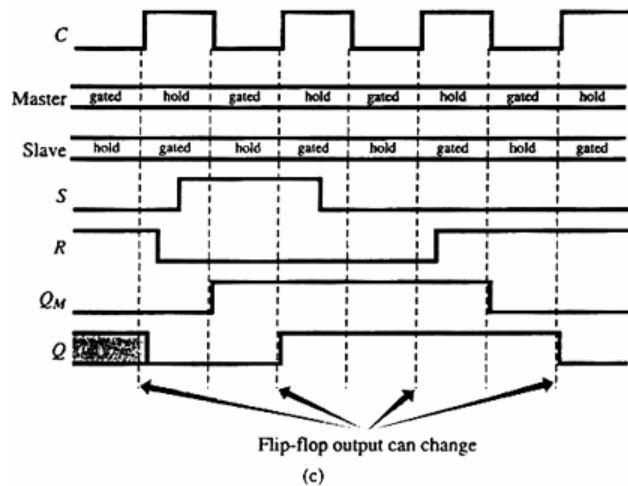  

16



# Flip-flop

- Master-Slave SR Flip-flop

S	R	Q	C	Q*
0	0	0		0 No change
0	0	1		1
0	1	0		0 Reset
0	1	1		0
1	0	0		1 Set
1	0	1		1
1	1	0		× Not allowed
1	1	1		×

$$Q^* = S + \bar{R}Q$$

(a)

# Flip-flop

- Master-Slave D Flip-flop

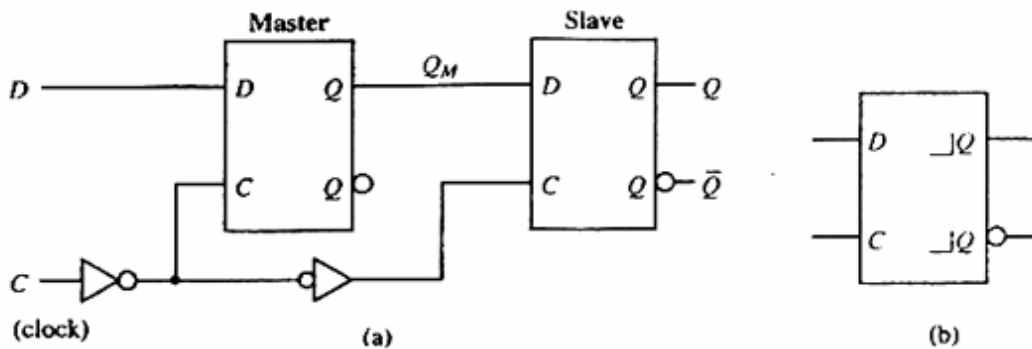




Figure 6.23 Master-slave D flip-flop. (a) Logic diagram. (b) Logic symbol.

# Flip-flop

$$Q^* = D$$

D	Q	C	Q*
0	0		0 Store 0
0	1		0
1	0		1 Store 1
1	1		1

(a)

  

(c)


Figure 6.24 Master-slave D flip-flop characteristics. (a) Excitation table. (b) State diagram. (c) Timing diagram.

# Flip-flop


## Master-Slave JK Flip-flop

J	K	Q	C	Q*
0	0	0		0 Hold
0	0	1		1
0	1	0		0 Reset
0	1	1		0
1	0	0		1 Set
1	0	1		1
1	1	0		1 Toggle
1	1	1		0

(a)

 




(b)

 

$$Q^* = \bar{K}Q + J\bar{Q}$$

# Flip-flop

- Master-Slave JK Flip-flop

   

21

# Flip-flop

- Edge-triggered D Flip-flop

- Called *positive edge triggered*, if it responds to a 0→1 clock transition.
- Called *Negative edge triggered*, if it responds to a 1→0 clock transition
- Special pin, *PRE* and *CLR*, for Asynchronous Set and Reset (without Clock).

22

# Flip-flop

- 7474 Dual Positive-edge-triggered D Flip-flop Module

Inputs				Outputs		Mode
$\overline{PRE}$	$\overline{CLR}$	D	CLK	Q	$\overline{Q}$	
L	H	x	x	H	L	Set
H	L	x	x	L	H	Clear
L	L	x	x	H	H	Not allow
H	H	H	$\uparrow$	H	L	Clocked open
H	H	L	$\uparrow$	L	H	Clocked open
H	H	x	L	$Q_0$	$\overline{Q}_0$	Hold


 


Figure 6.29 SN7474 excitation table  
Book Volume 2, Texas Instruments Inc.,


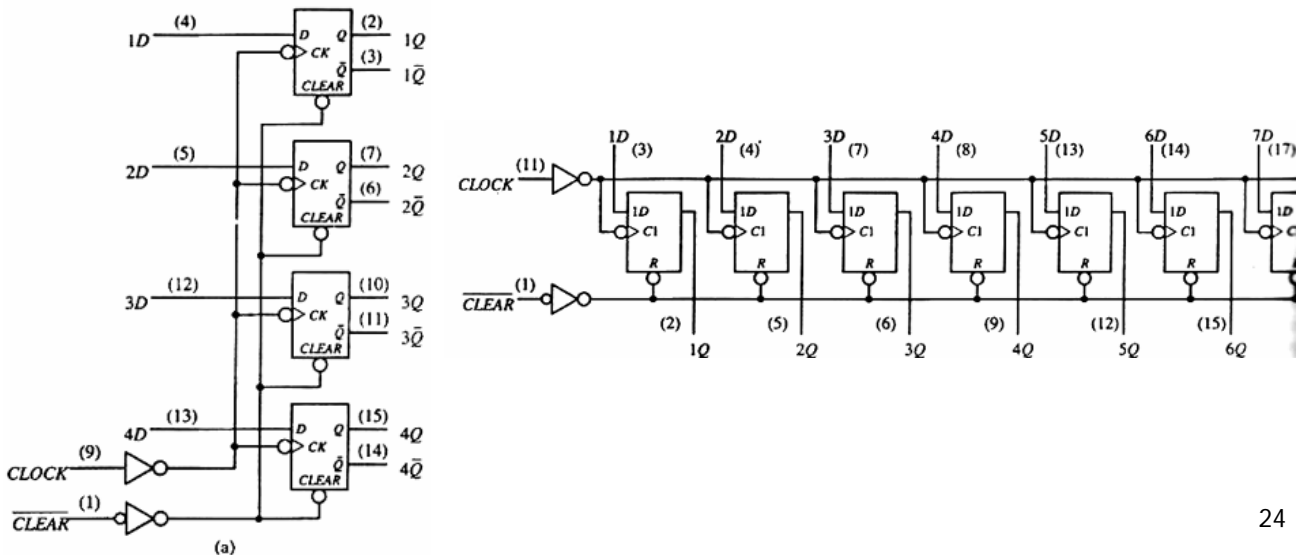
# Flip-flop

- 74175 and 74273 Dual Positive-edge-triggered D Flip-flop Module


  
# Flip-flop

- 7473 Dual Positive-edge-triggered JK Flip-flop Module




# Flip-flop

- Edge-triggered T (trigger or toggle) Flip-flop
  - Used in sequential logic circuit that counts pulse on a signal line.

T	Q	Q*	
↓	0	1	Toggle
↓	1	0	Toggle


(a)

 


(b)

$$Q^* = \bar{Q}$$

Figure 6.34 Edge-triggered T flip-flop characteristics  
(a) Excitation table. (b) State diagram.

 


(a)

 

(b)


# Flip-flop

## ■ Clocked T Flip-flop

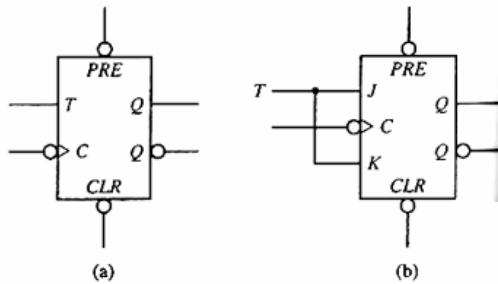

$$Q^* = J\bar{Q} + \bar{K}Q$$

$$= T\bar{Q} + \bar{T}Q$$

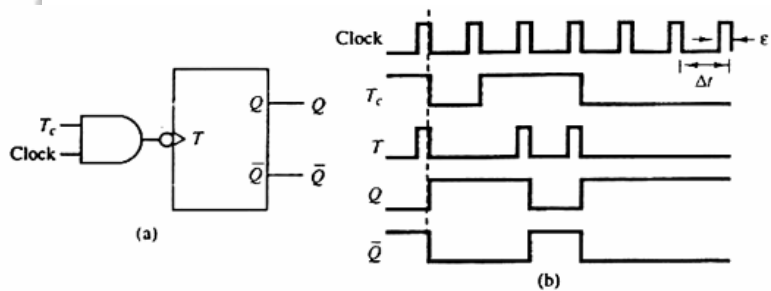

27

# Flip-flop

## ■ Latch and Flip-flop Summary

**TABLE 6.3 SUMMARY OF LATCH AND FLIP-FLOP CHARACTERISTICS**

Device	Characteristic Equation
SR latch	$Q^* = S + \bar{R}Q$
Gated SR latch	$Q^* = SC + \bar{Q}R + \bar{C}Q$
D latch	$Q^* = DC + \bar{C}Q$
SR flip-flop	$Q^* = S + \bar{R}Q$
D flip-flop	$Q^* = D$
JK flip-flop	$Q^* = \bar{R}Q + J\bar{Q}$
T flip-flop (edge-triggered)	$Q^* = \bar{Q}$
T flip-flop (clocked)	$Q^* = T\bar{Q} + \bar{T}Q$

28